

**African Centre for
Advanced Studies**

**National Advanced School of
Engineering, UYI**

ELECTRIC AND ELECTRONIC CIRCUITS

PHY 225

Dr. DIDIER BELOBO BELOBO

Transistors

Overview

Introduction

Bipolar junction transistors, transistor effect, characteristics; polarization, operating point, temperature stabilization

Field effect transistor

Junction field effect transistor

Insulated gate field effect transistor

Transistors I: BJTs

Introduction

December 23 afternoon at Bell Telephone Laboratories, 1947, Walter H. Brattain and John Bardeen and William Schockley demonstrated the amplifying action of the first transistor

In 1951, William B. Schockley invented the first junction transistor, a semiconductor device that can amplify (enlarge) electronic signals such as radio and television signals

Transistors I: BJTs

Introduction



Fig. 1 First transistor

1956, **physics Nobel** prize received by Brattain, Bardeen Schockley for ‘**their research on semiconductors and the discovery of the transistor effect**’

Transistors

Introduction

Applications of transistors

Current regulation

Switching signals



Amplification of
an input signal

in lcs are found
everywhere

Transistor: BJTs

A BJT: semiconductor doped to obtain a series of two opposite junctions. 2 types exist: NPN and PNP

NPN BJT

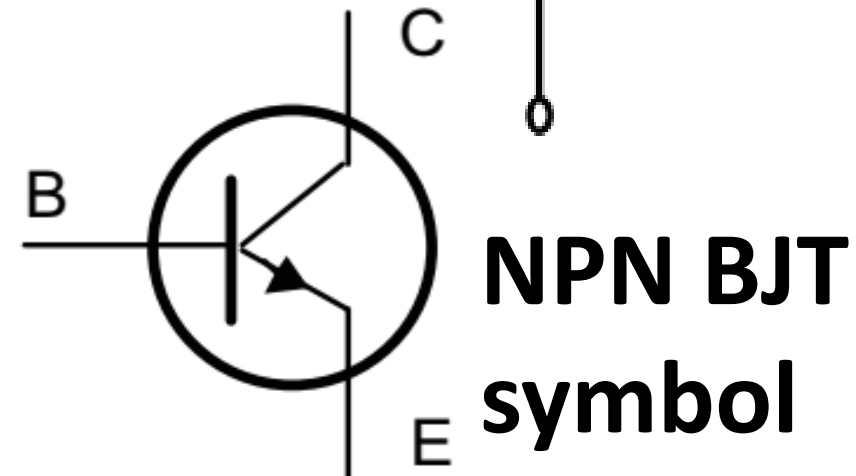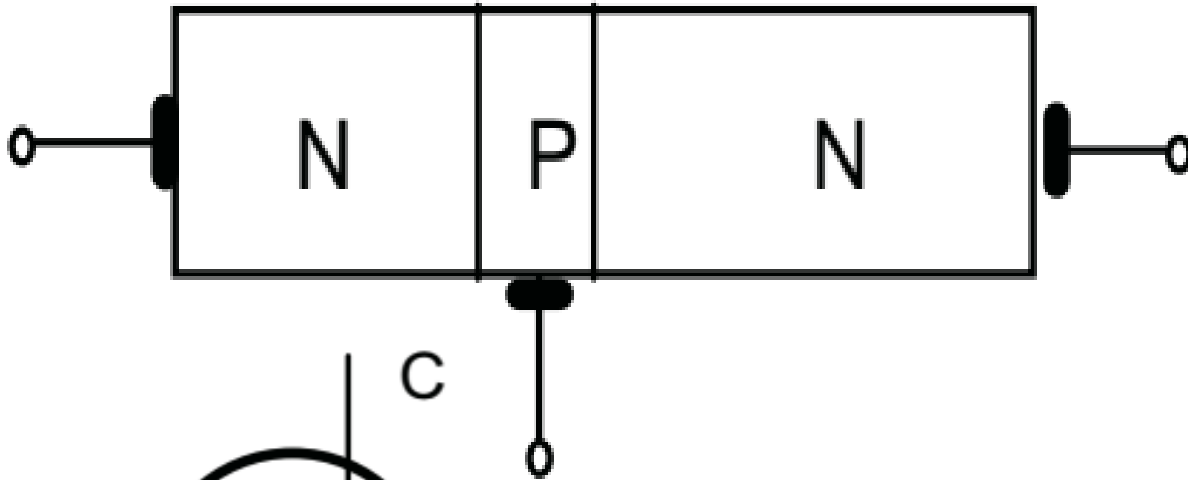

PNP BJT

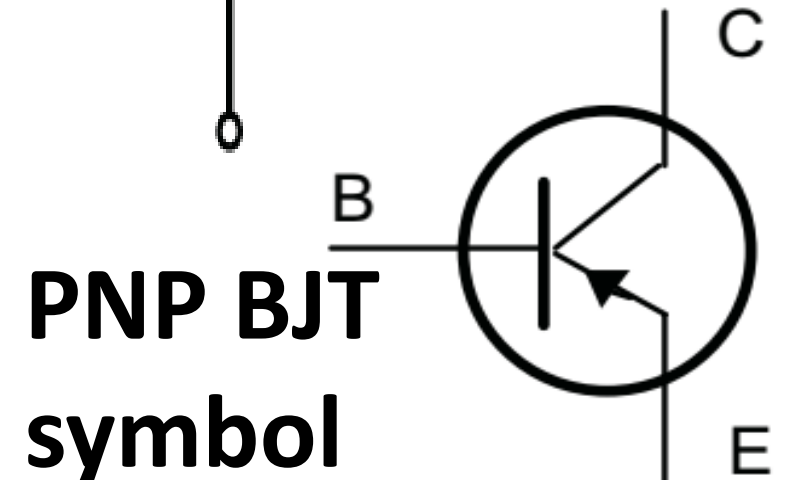
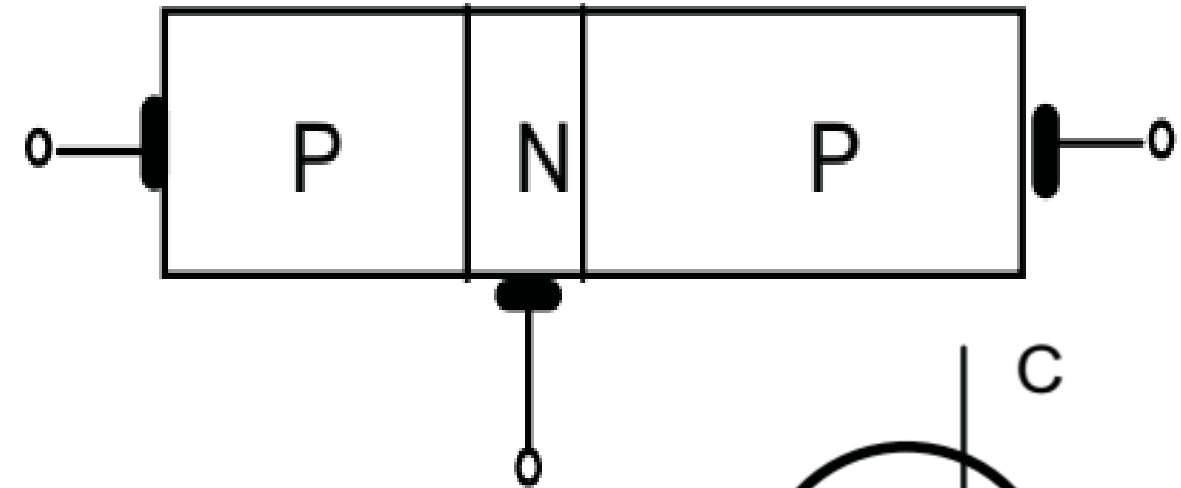


Fig. 2

Transistors: focused NPN BJTs

Unbias transistor

collector
intermediate
doping

base
lightly doped

emitter
heavily doped

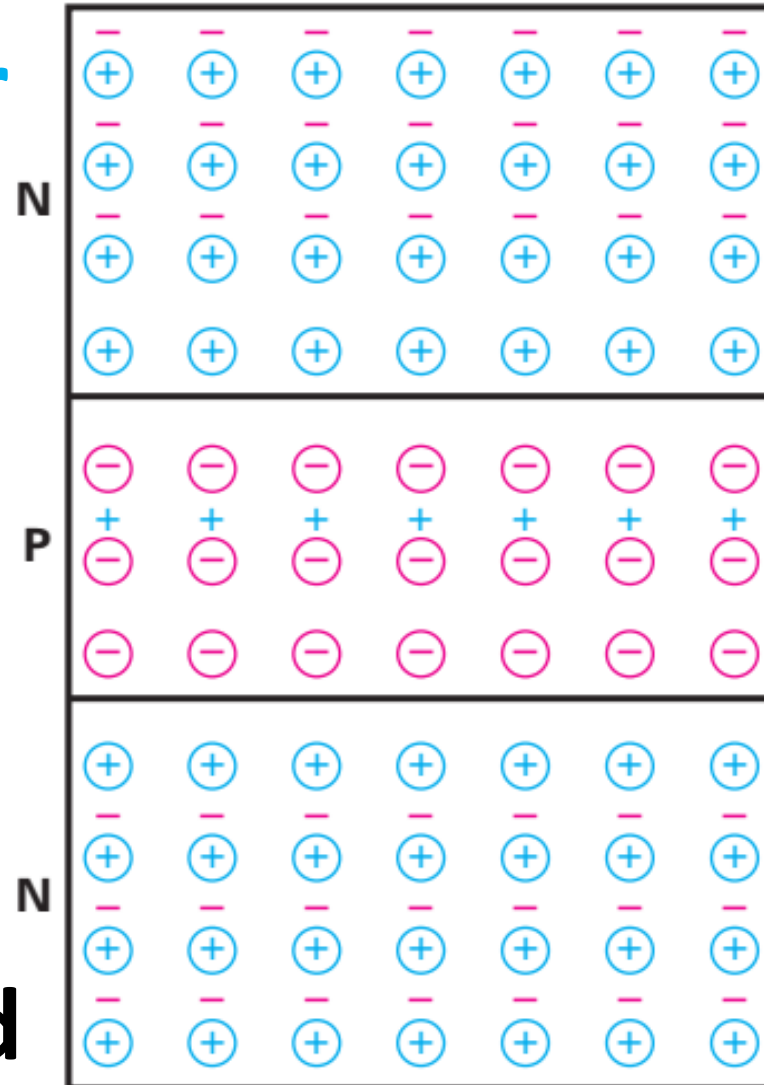


Fig. 3

base much thinner
than collector and
emitter regions

$$V_0 = 0.7 \text{ V}$$


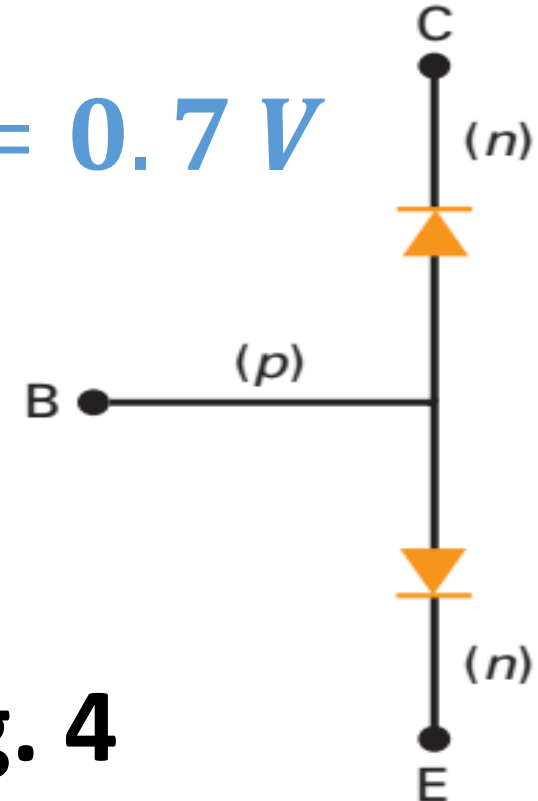


Fig. 4

Transistors: focused NPN BJTs

bias transistor

Fig. 5

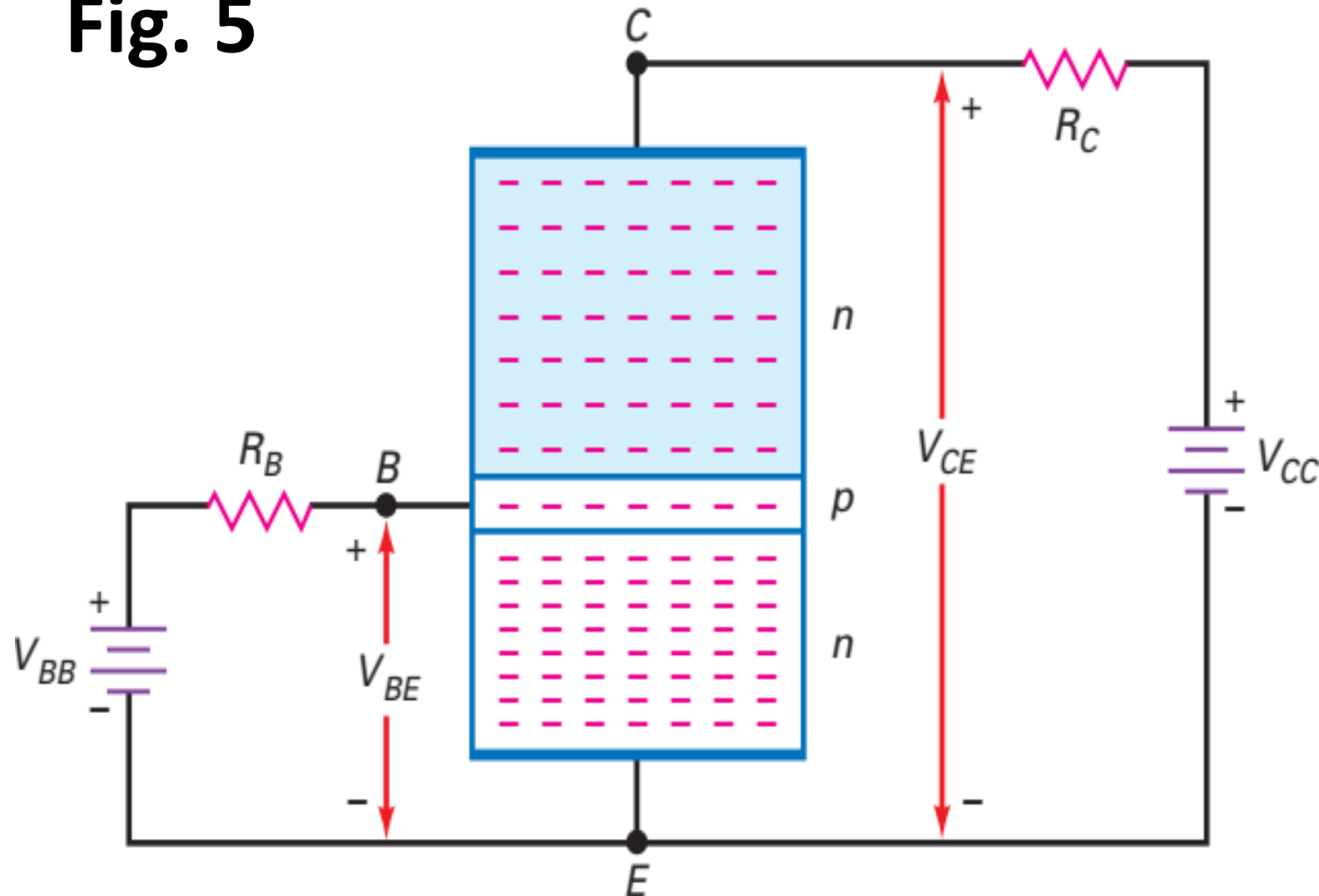

V_{BB} : forward biases
emitter diode

V_{CC} : reverse biases
collector diode

Transistors: focused NPN BJTs

bias transistor

Emitter role: injects its free e^- into the base

Base role: pass emitter-injected e^- on to the collector

Collector role: collects most of all free e^- from the base


Free e^- from emitter diffuse to the base, few recombine with holes, most cross the base as the latter width is small, free e^- in collector feel the attraction of V_{CC} , flow through the collector and enter the circuit

Transistors: focused NPN BJTs

BJT currents

Fig. 6

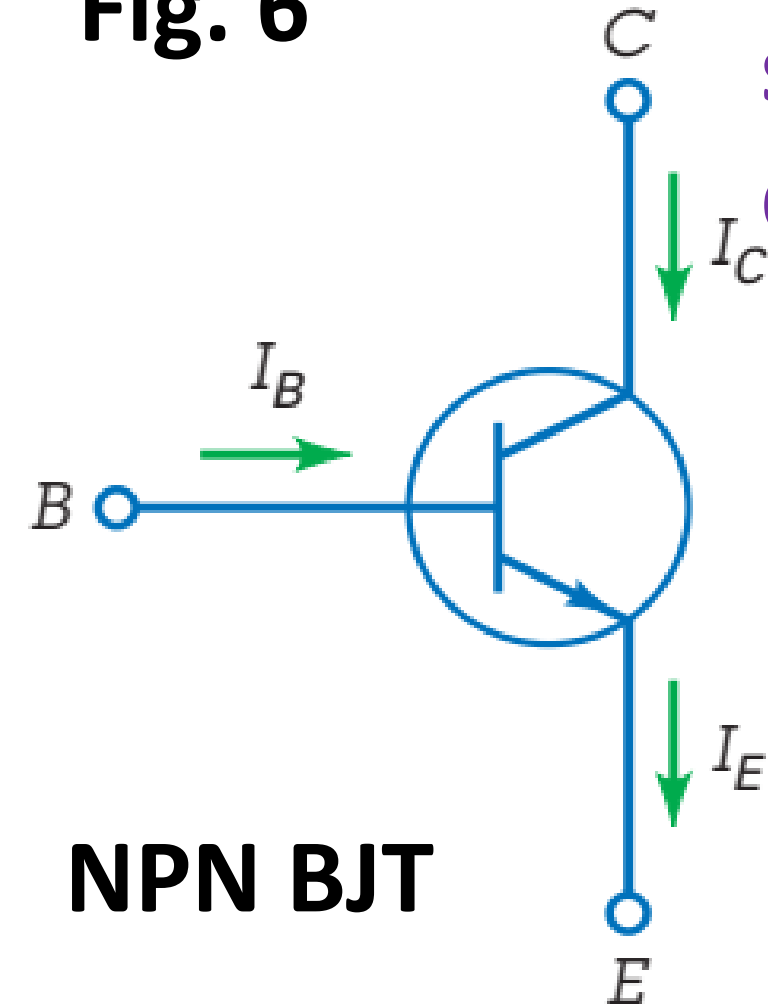solid line arrows: current flows
dashed line arrows: e^- flows




NPN BJT

I_C : collector current

I_B : base current

I_E : emitter current

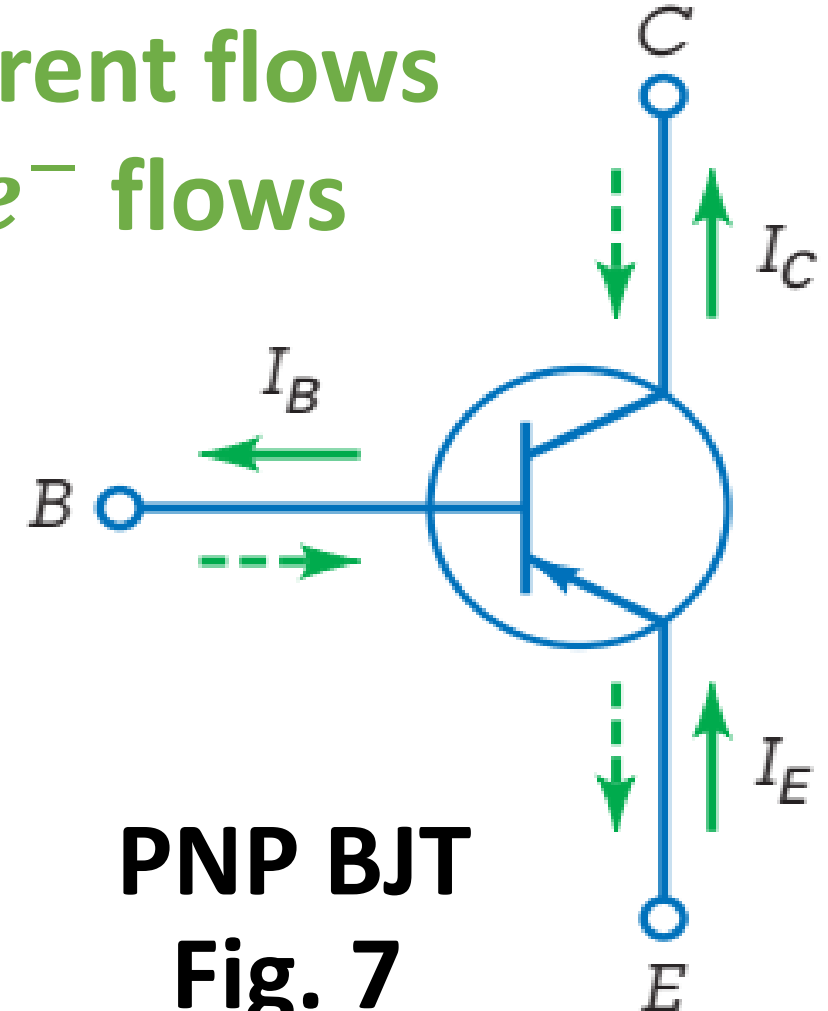

PNP BJT

Fig. 7

Transistors: focused NPN BJTs

BJT currents

Kirchoff law: $I_E = I_C + I_B$ Eq.(1)

α : proportion of free e^- injected from emmitter that arrive to the collector, typically $0.95 \leq \alpha \leq 0.99$

$$I_C = \alpha I_E \quad \text{Eq.(2)}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B \quad \text{Eq.(3)}$$

Transistors: focused NPN BJTs

BJT currents

$$\beta = \frac{\alpha}{1 - \alpha} \quad \text{Eq.(4)} \quad \beta \text{ is very large as } \alpha \text{ tends to } 1$$

Transistor
effect

$$I_C = \beta I_B \quad \text{Eq.(5)}$$

Eq.(5) means that from a small base current, one obtains an amplified collector current, a phenomenon known as **the transistor effect**

Transistors: focused NPN BJTs

BJT currents

Examples:

- 1) A transistor has a collector current of 10 mA and a base current of 40 μA . What is the current gain of the transistor?
- 2) A transistor has a current gain of 175. If the base current is 0.1 mA, what is the collector current?

Transistors: focused NPN BJTs

BJT characteristics

3 ways to connect a transistor: (a) CE (common emitter), (b) CC (common collector), or (c) CB (common base)


Common here is understood as connection to the common or ground of each source voltage

We focus on CE connection that is widely used with

Transistors: focused NPN BJTs

BJT characteristics

Fig. 8

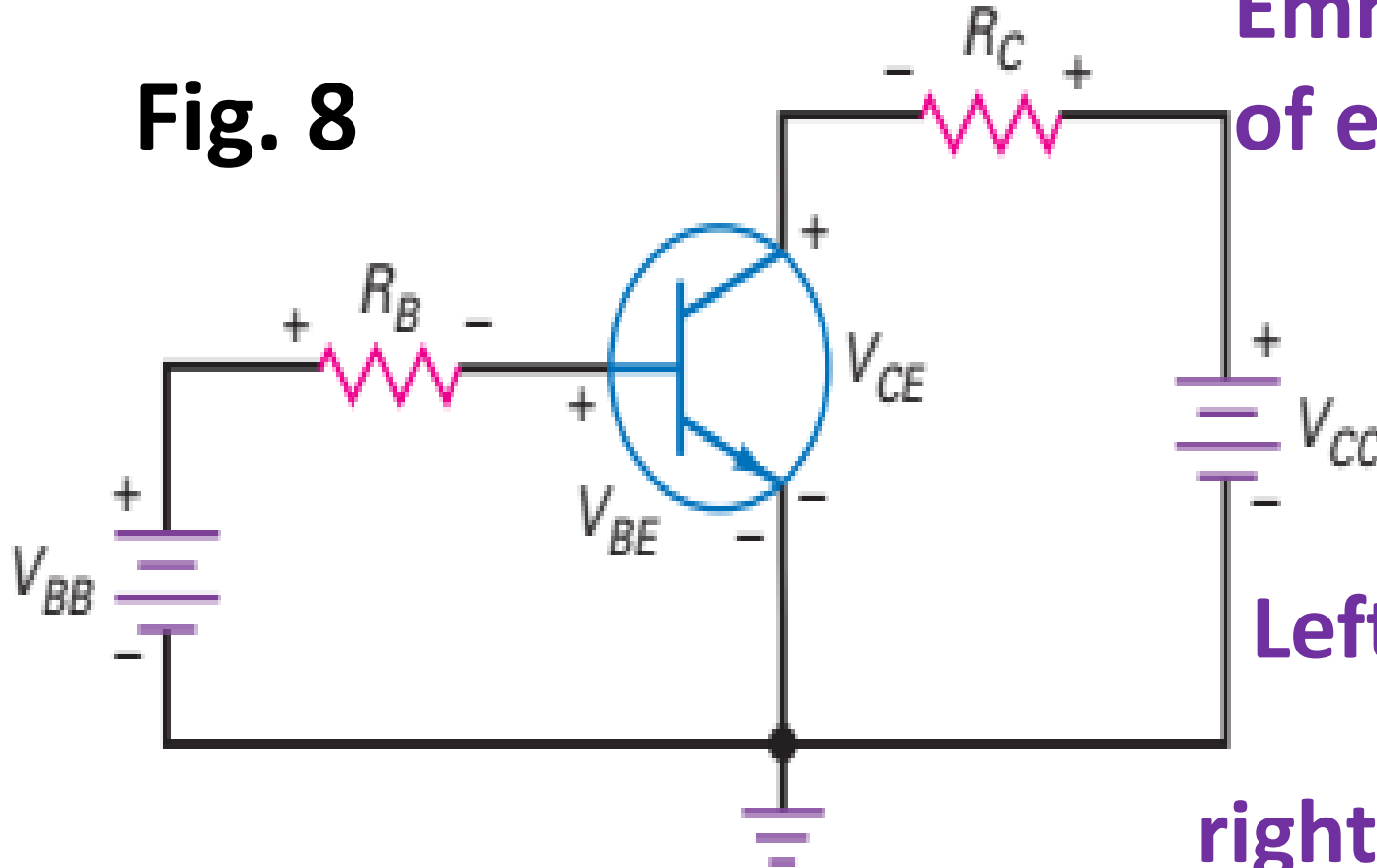

Emmitter connected to ground
of each source voltage

Left loop referred to as input

right loop referred to as output

Transistors: focused NPN BJTs

BJT characteristics

Notations

Double subscripts: same subscripts mean source voltage: V_{BB} base voltage source, V_{CC} collector voltage source; different subscript mean voltage between 2 points: V_{BE} voltage between base and emitter

single subscripts mean node voltage or voltage between the subscripted point and the ground: $V_C = V_C - V_E = V_{CE}$

Transistors: focused NPN BJTs

BJT characteristics

Base characteristics

Emitter diode, same current vs voltage curve, choose approximation

Fig. 9

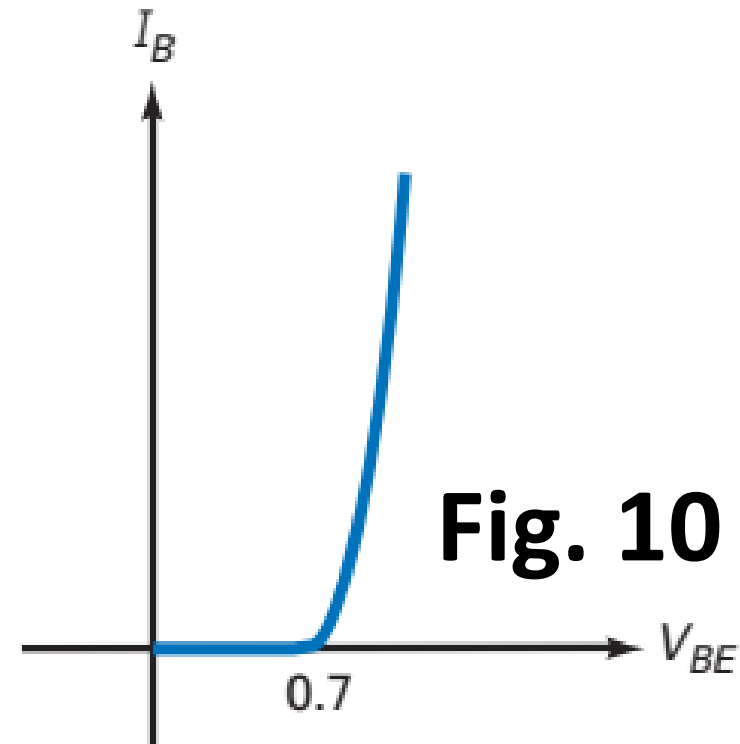
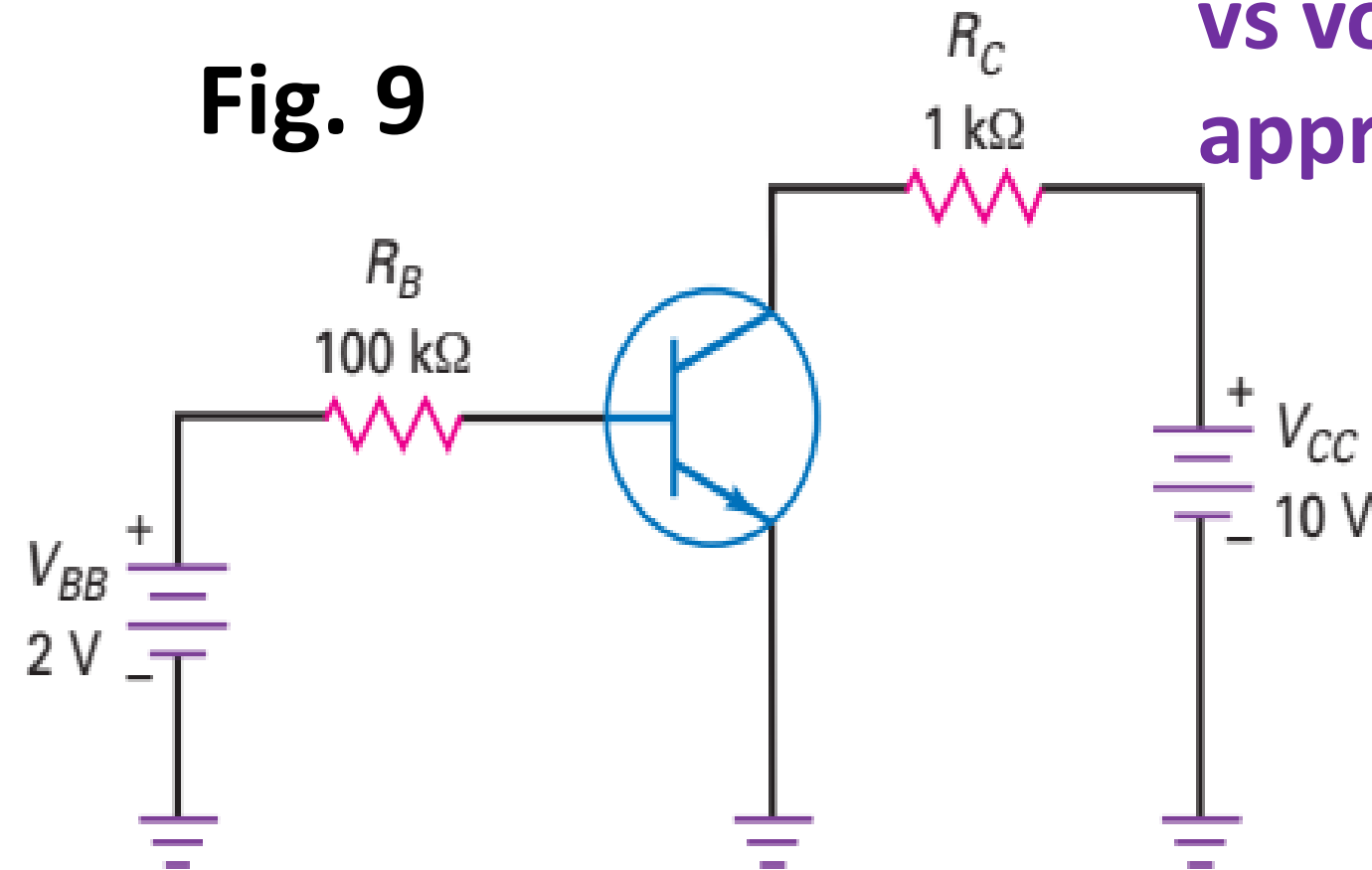


Fig. 10

Transistors: focused NPN BJTs

BJT characteristics

Base characteristics

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad \text{Eq.(6)}$$

example

Use the second approximation to calculate the base current in Fig. 9. What is the voltage across the base resistor? The collector current if $\beta = 200$?


Transistors: focused NPN BJTs

BJT characteristics

collector characteristics

small increase of V_{CE} , sharp increase of I_C up

Fig. 11 to a stable value of 1 mA

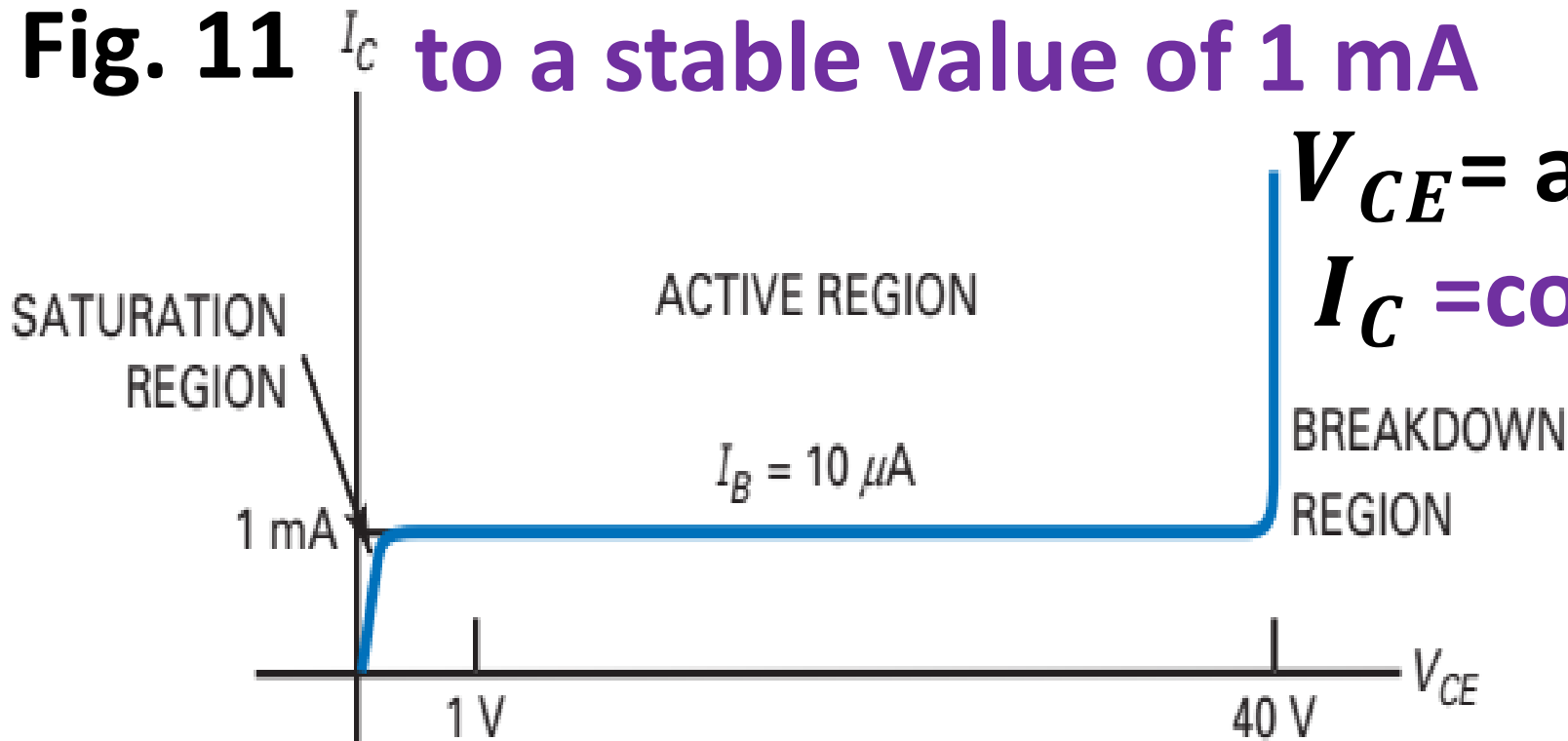

V_{CE} = a few tens of 1 V-40 V,
 I_C = constant = 1 mA

$V_{CE} = 0 \text{ V}$, collector not reverse bias, $I_C = 0 \text{ A}$

Transistors: focused NPN BJTs

BJT characteristics

collector characteristics

$V_{CE} > 40$ V, collector breaks down, transistor effect lost
Constant region in Fig. 10 means further increase of V_{CE} cannot increase I_C as it is due only to free e^- from the base

Collector voltage: $V_{CE} = V_{CC} - R_C I_C$ Eq.(7)

Power dissipation: $P_D = V_{CE} I_C$ Eq.(8)

Power dissipation heats up the transistor may damaging it

Transistors: focused NPN BJTs

BJT characteristics

collector characteristics

Regions of operation

Active region: I_C constant, transistor in normal operation

Saturation region: early rising part of the curve, V_{CC} is insufficient to collect all free e^- from the base, $I_B > I_C$

Breakdown region: almost vertical part of curve, transistor gets damage in this region


Transistors: focused NPN BJTs

BJT characteristics

collector characteristics

Regions of operation

Fig. 12

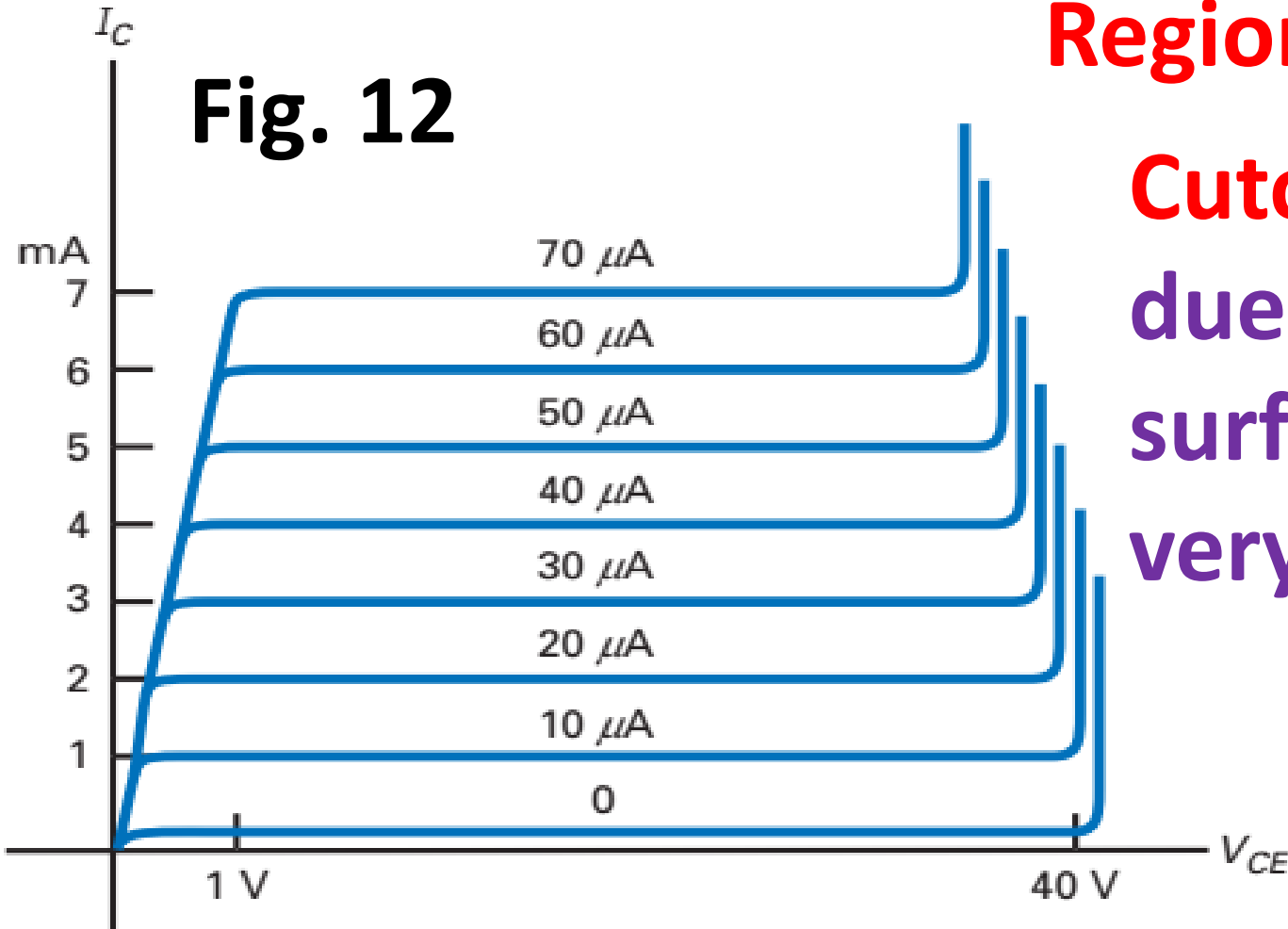


Cutoff region: $I_B = 0 \text{ A}$, $I_C \neq 0$
due to minority carriers and
surface leakage current, I_C is
very small orders of 50 nA

Transistors: focused NPN BJTs

BJT characteristics

collector characteristics

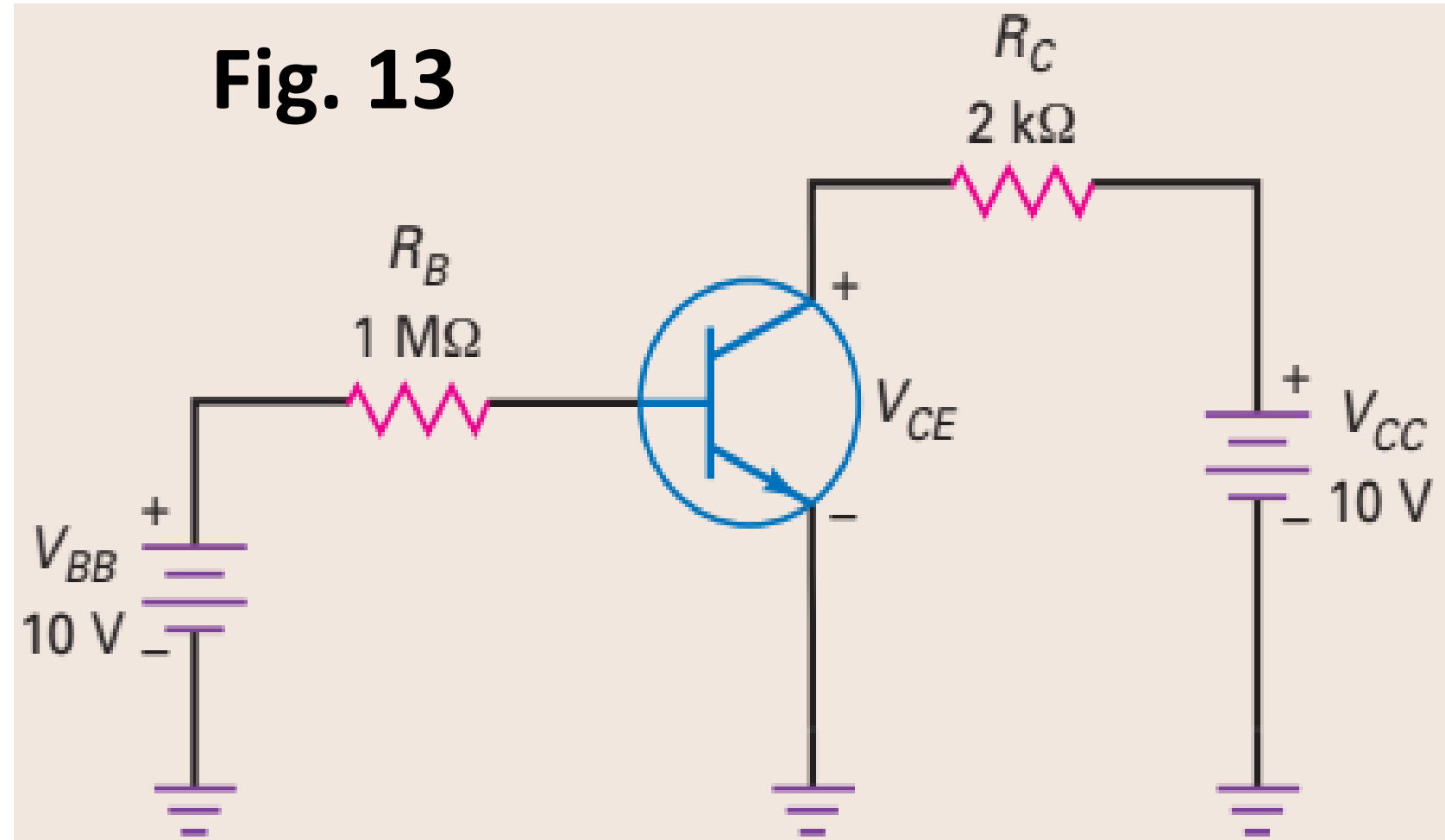Example: what
are I_B , I_C , V_{CE}
and P_D ?



Transistors: focused NPN BJTs

BJT characteristics

Transistor approximations

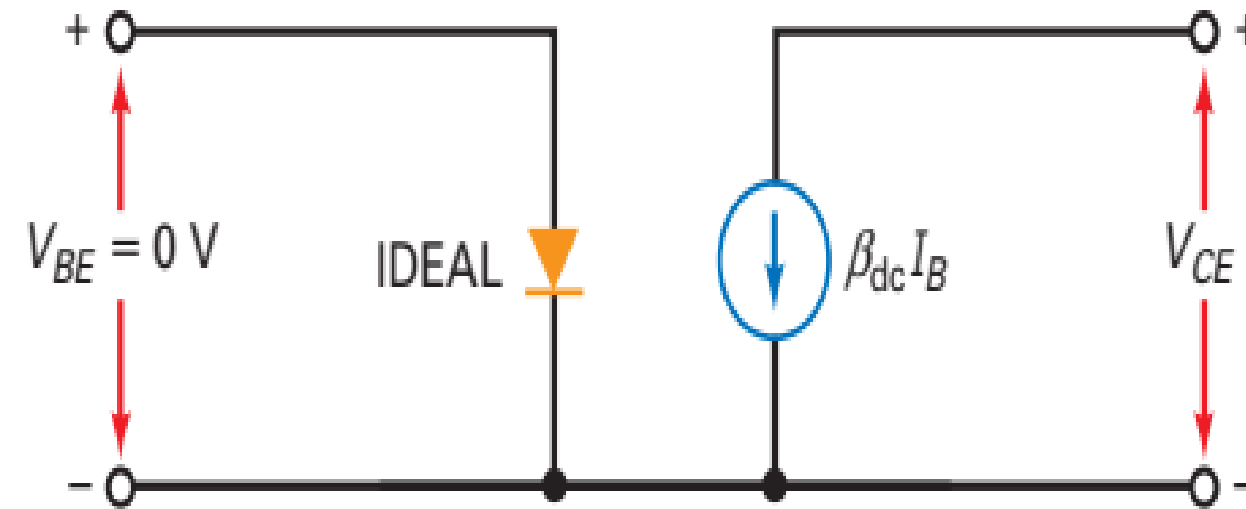


Fig. 14

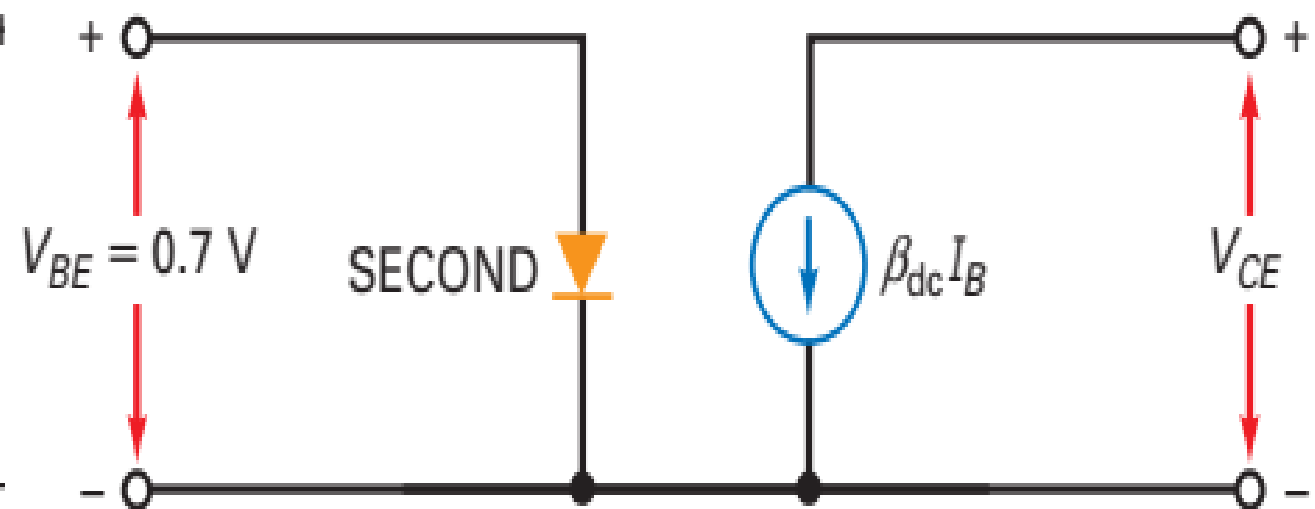


Fig. 15


Transistors: focused NPN BJTs

BJT characteristics

Transistor approximations

Example: what is V_{CE} ? Use first the ideal and second degrees approximations


Fig. 16

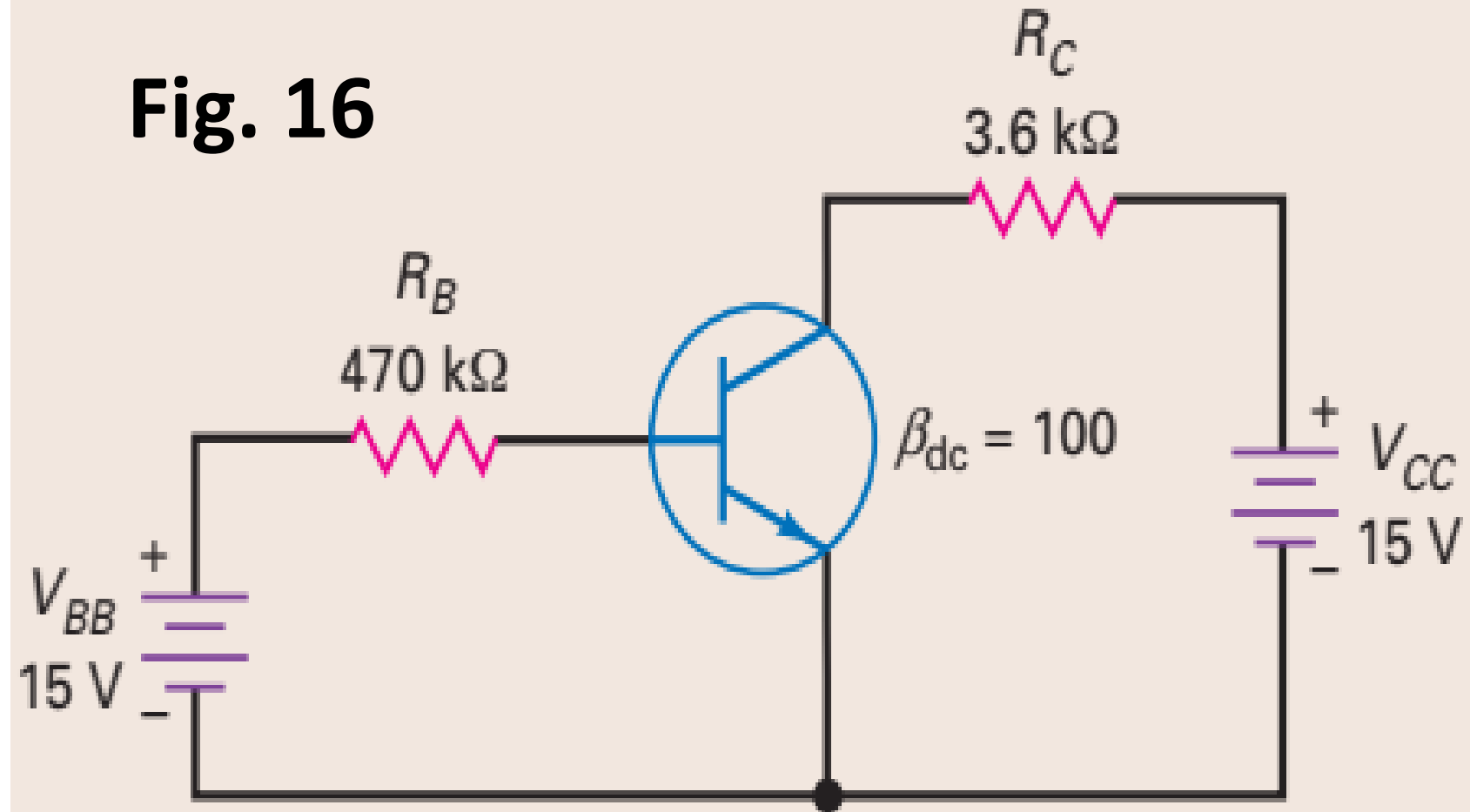

Transistors: focused NPN BJTs

BJT characteristics

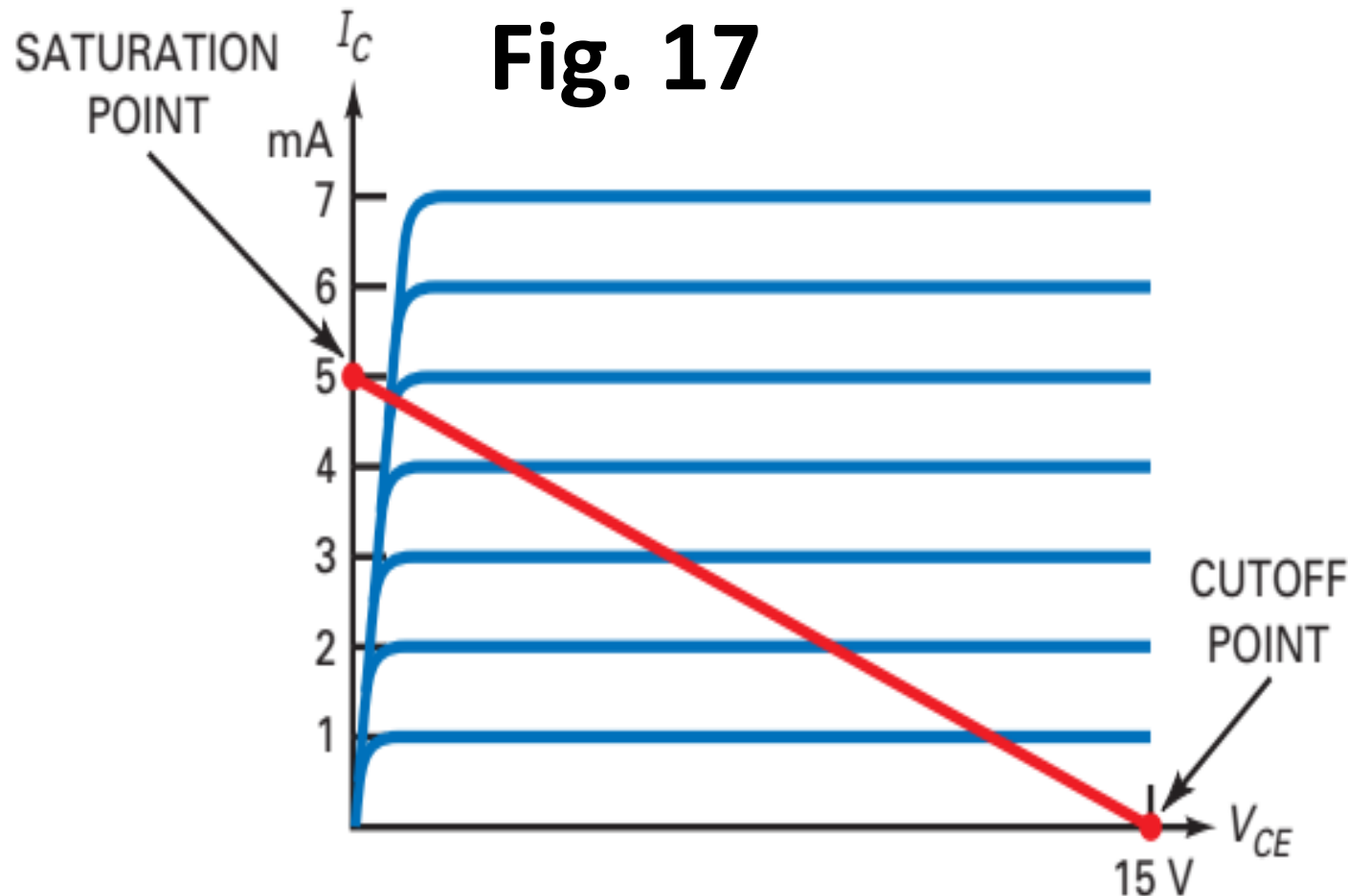Load line: base bias case, i.e., base current fixed




$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \quad \text{Eq.(9)}$$

Load line contains all possible operating points of the transistor

Transistors: focused NPN BJTs

BJT characteristics

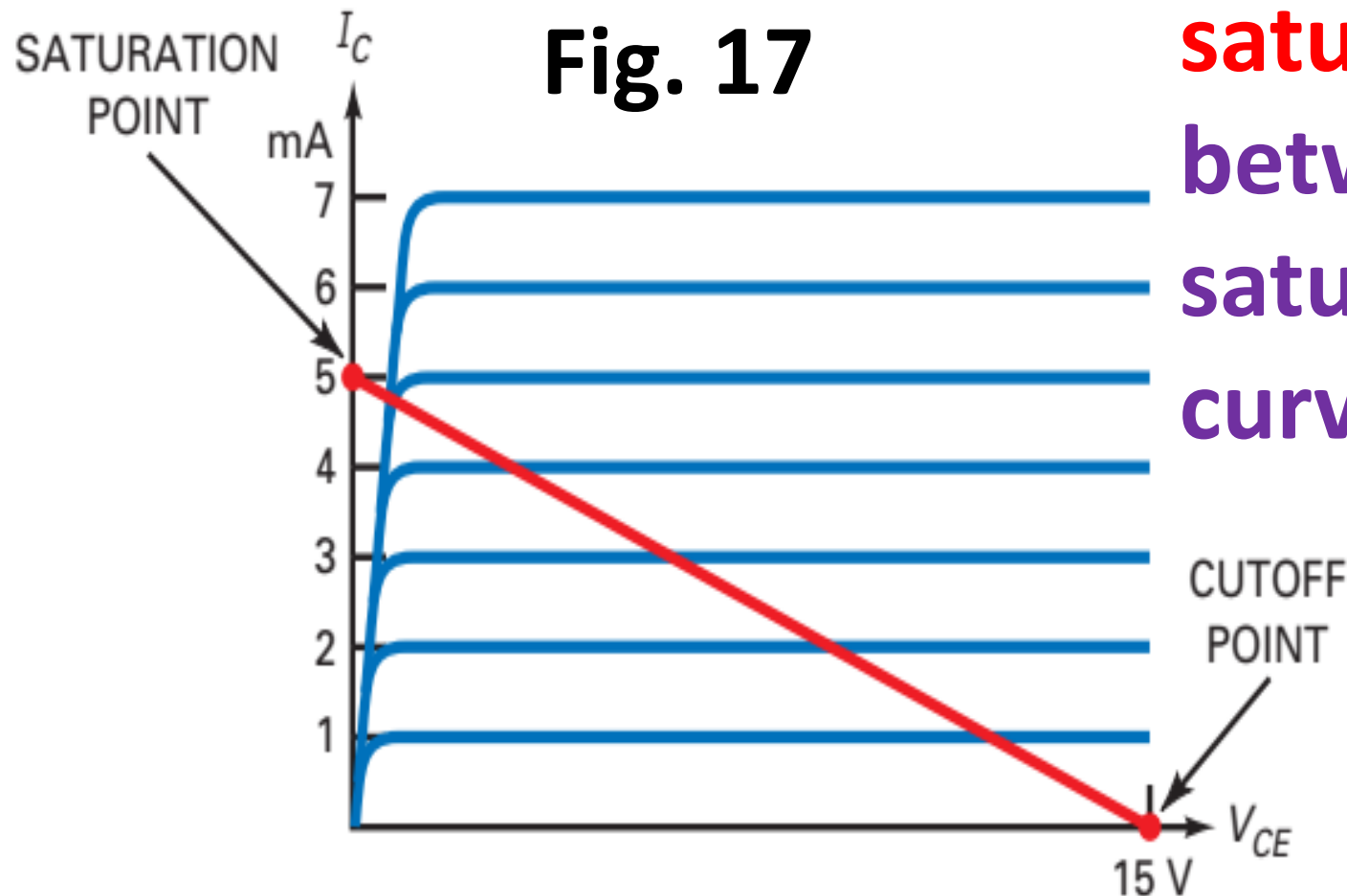Load line: base bias case, i.e., base current fixed




saturation point: intersection between load line and saturation region of collector curves, $V_{CE} \approx 0$ V.

$$I_{CS} \approx \frac{V_{CC}}{R_C} \quad \text{Eq.(10)}$$

Transistors: focused NPN BJTs

BJT characteristics

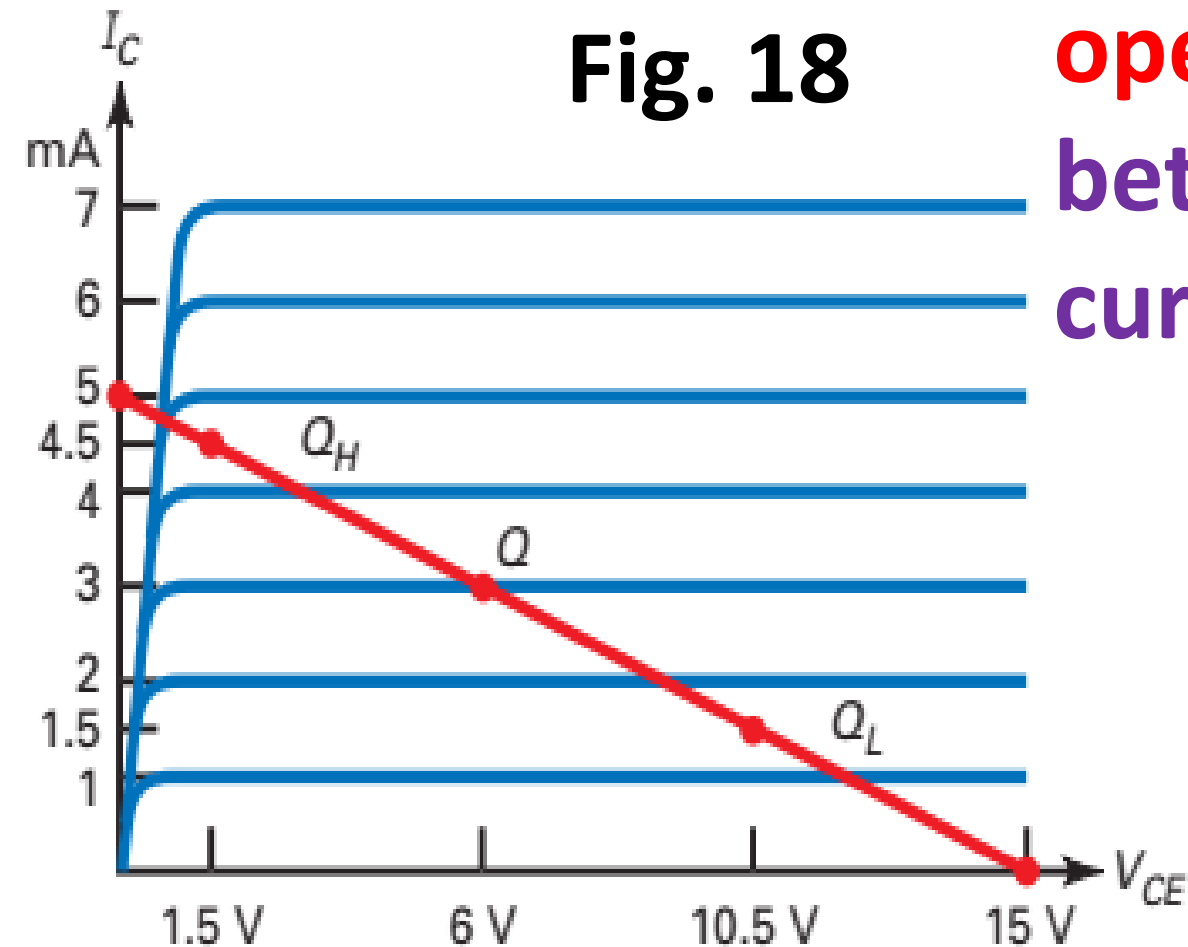Load line: base bias case, i.e., base current fixed



operating point Q : intersection
between load line and $I_C (V_{CE})$
curve $Q(I_C, V_{CE})$

$$I_B = \frac{(V_{BB} - V_{BE})}{R_B} (V_{CE})$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CE} - R_C I_C$$

Transistors: focused NPN BJTs

BJT characteristics

Recognize saturation

1. Assume transistor operating in active region.
2. Carry out the calculations for currents and voltages.
3. If an impossible result occurs in any calculation, the assumption is false.

Transistors: focused NPN BJTs

BJT characteristics


Recognize saturation

example

Fig. 19


a) Compute I_B and I_C , conclude

b) Compute I_C and V_{CE} , conclude

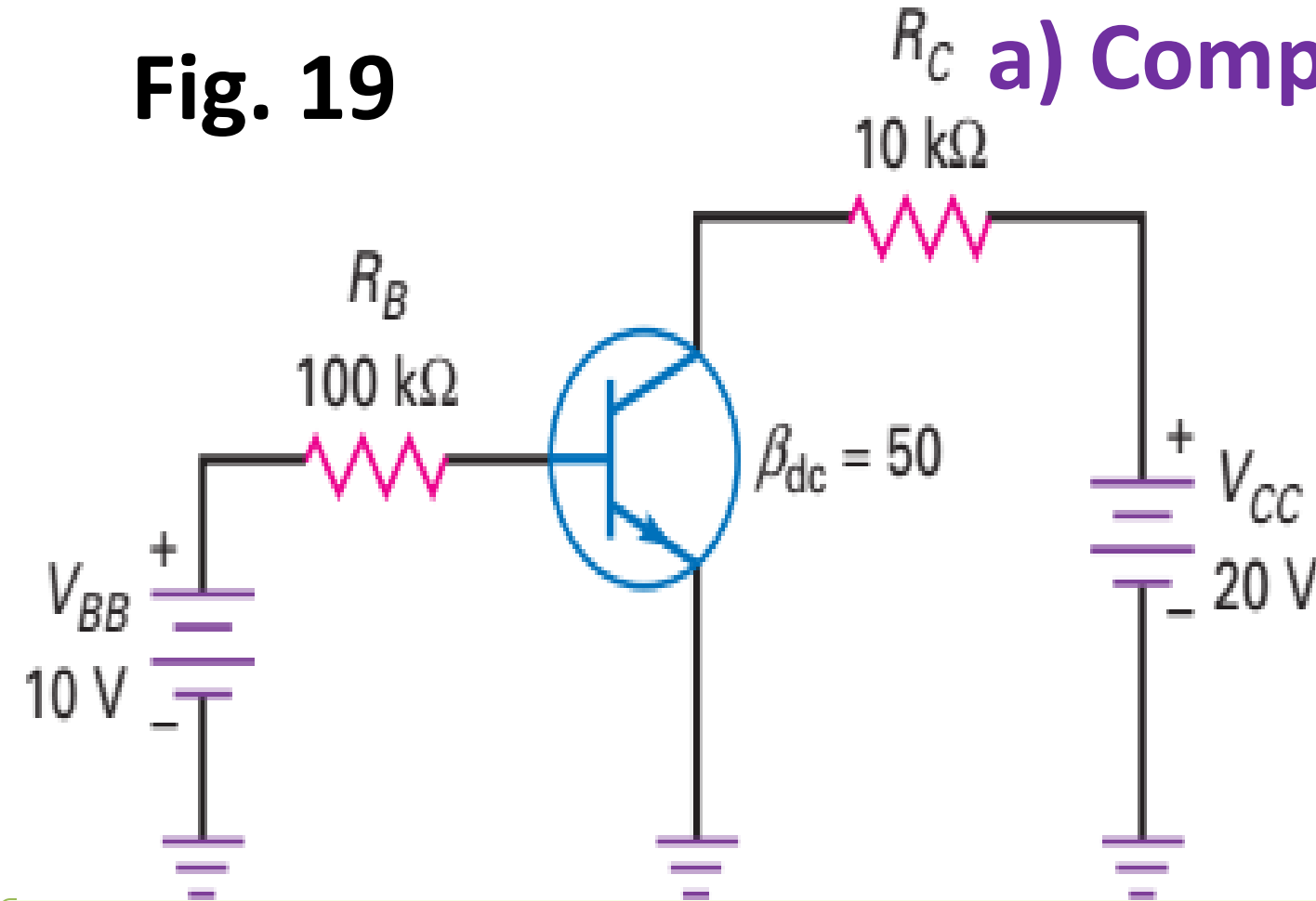

Transistors: focused NPN BJTs

Fig. 20

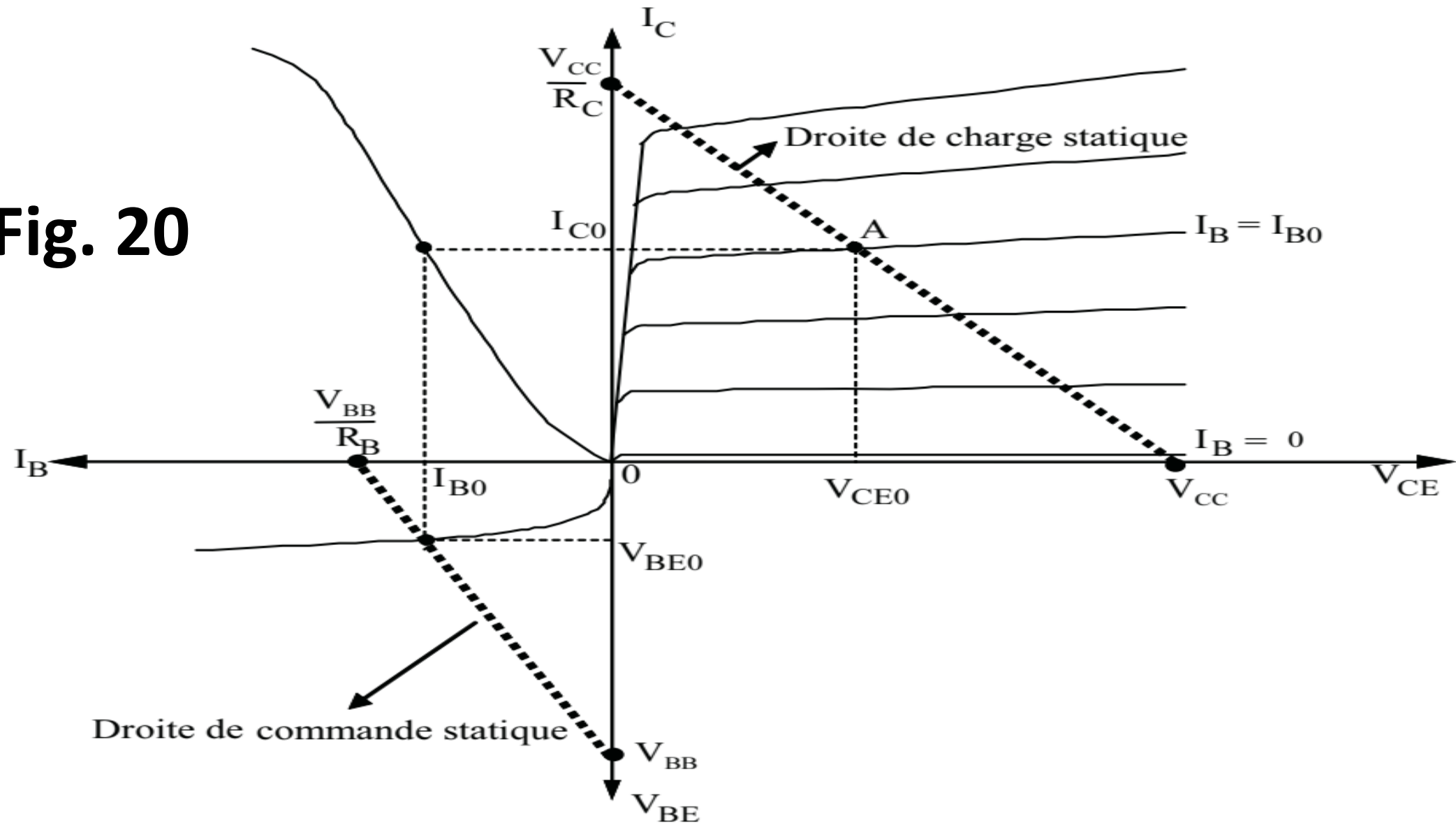

Transistors: focused FETs

Introduction

Field effect transistor (FET): unipolar device as current is due only one type of charge carriers (e^- or holes)

Advantages of FETs over BJTs

high input impedance

voltage controlled device

high degree of isolation

less noisy effect

between input and output

Transistors: focused FETs

Introduction

Types of FETs

**(a) Junction FET
(JFET)**

**(b) Metal oxide semiconductor
FET (MOSFET)**

Transistors: focused FETs

Junction field effect transistor (FET)

JFET: four-terminal device, terminal names: drain, gate, source, and body always connected to the source

Types of JFET

Fig. 21 N-channel JFET


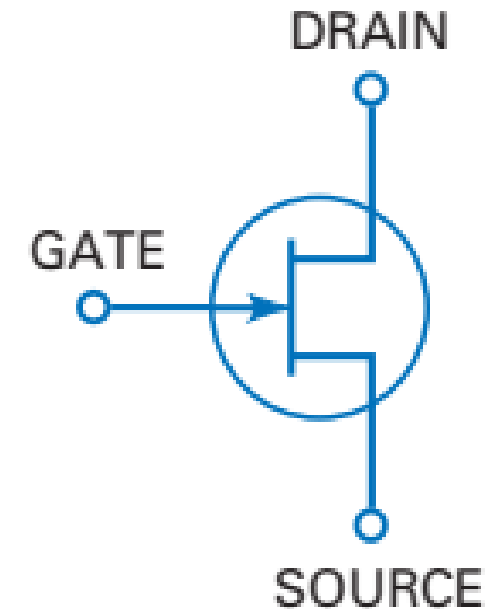


Fig. 22 P-channel JFET


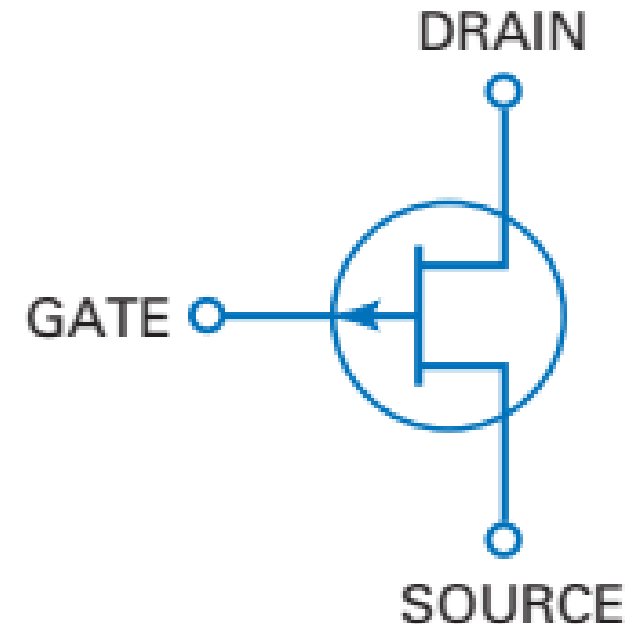


Transistors: focused FETs

Junction field effect transistor (FET)

Construction of JFET

Fig. 24 P-channel JFET

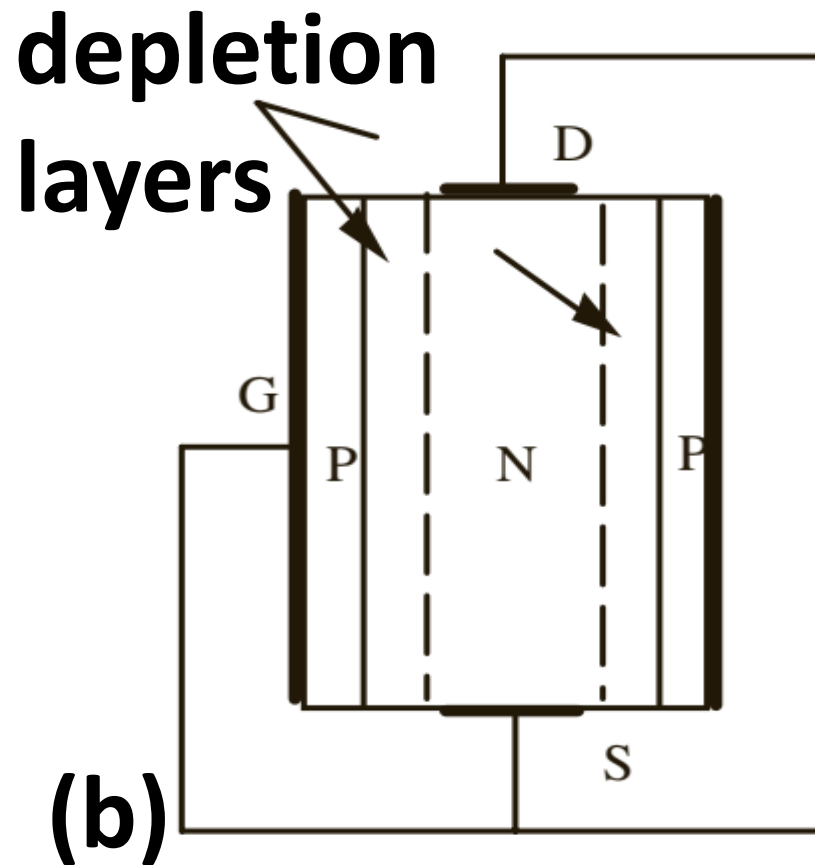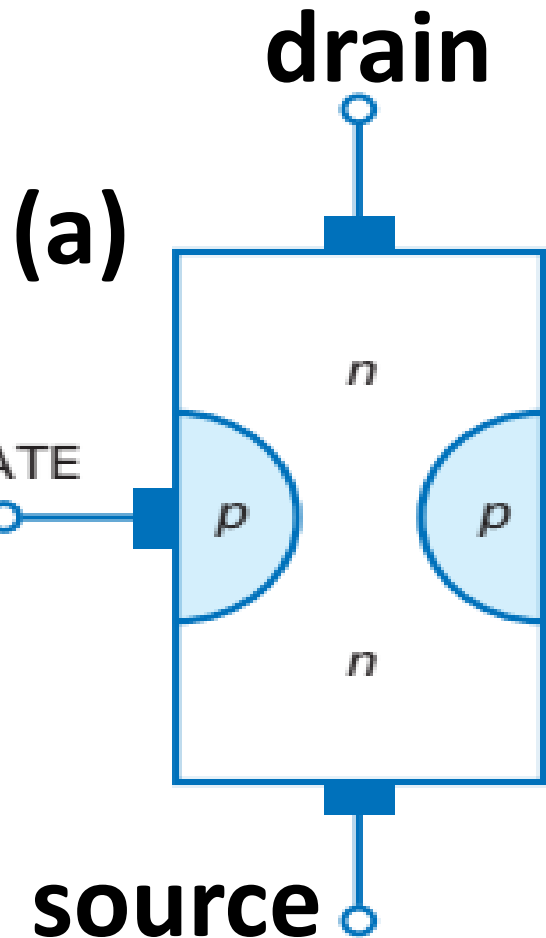

P-regions are internally connected to get one gate lead

Term field effect related to the presence of two depletion layers


charge carriers are e^-

Transistors: focused FETs


Junction field effect transistor (FET)

Construction of JFET

Fig. 25 P-channel JFET

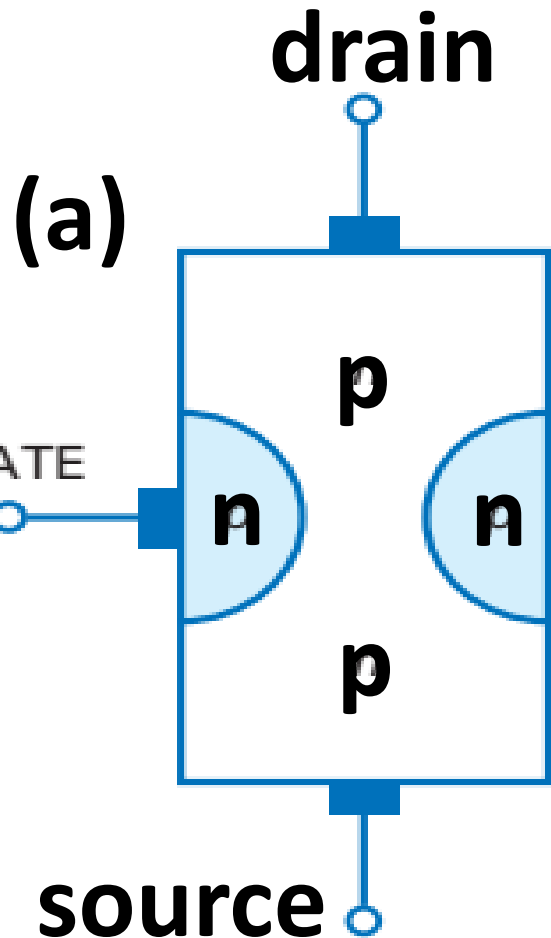

depletion
layers

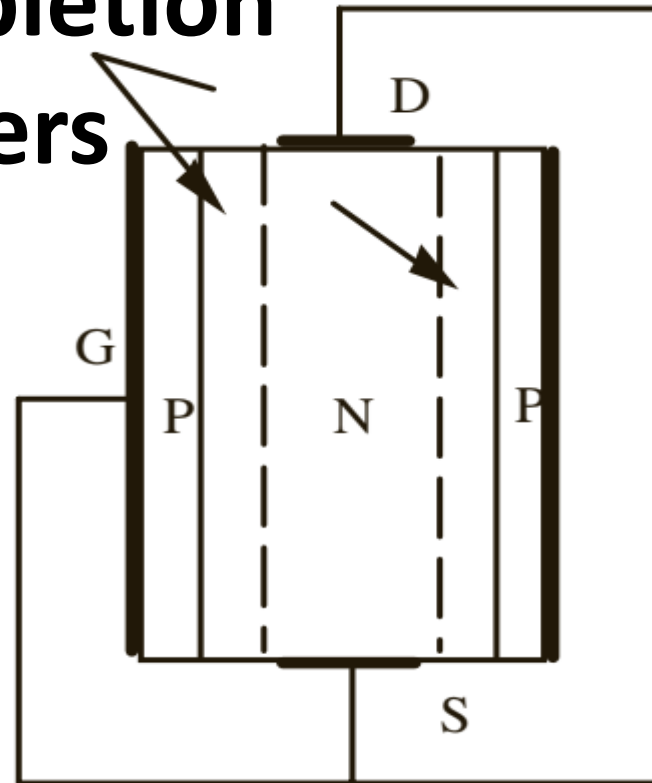


charge carriers are
holes

(b)

Transistors: focused FETs

Junction field effect transistor (FET) working of JFET

Fig. 26 Normal biasing a JFET

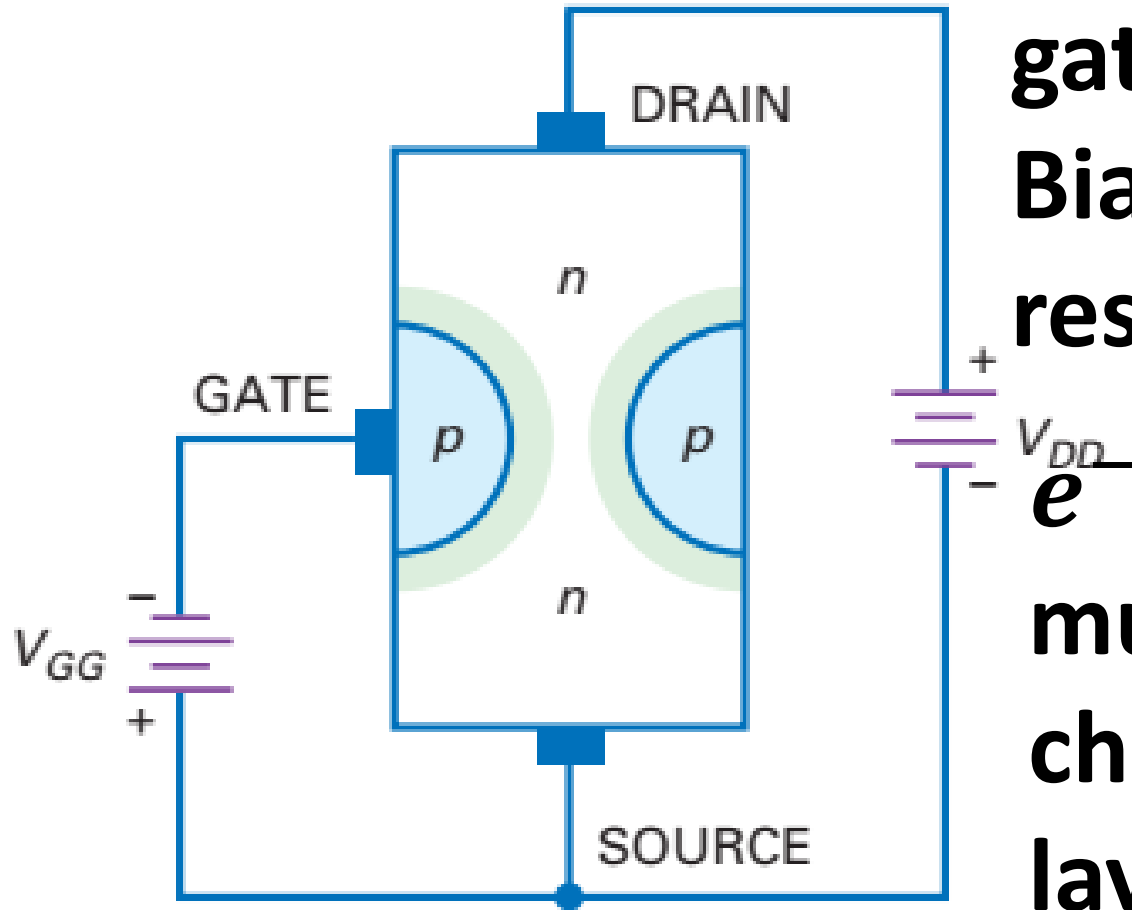


gate-source diode always reverse
Bias, Gate current $I_G \approx 0$, input
resistance almost infinite

e^- flowing from source to drain
must pass through narrow
channel between the depletion
layers.

Transistors: focused FETs

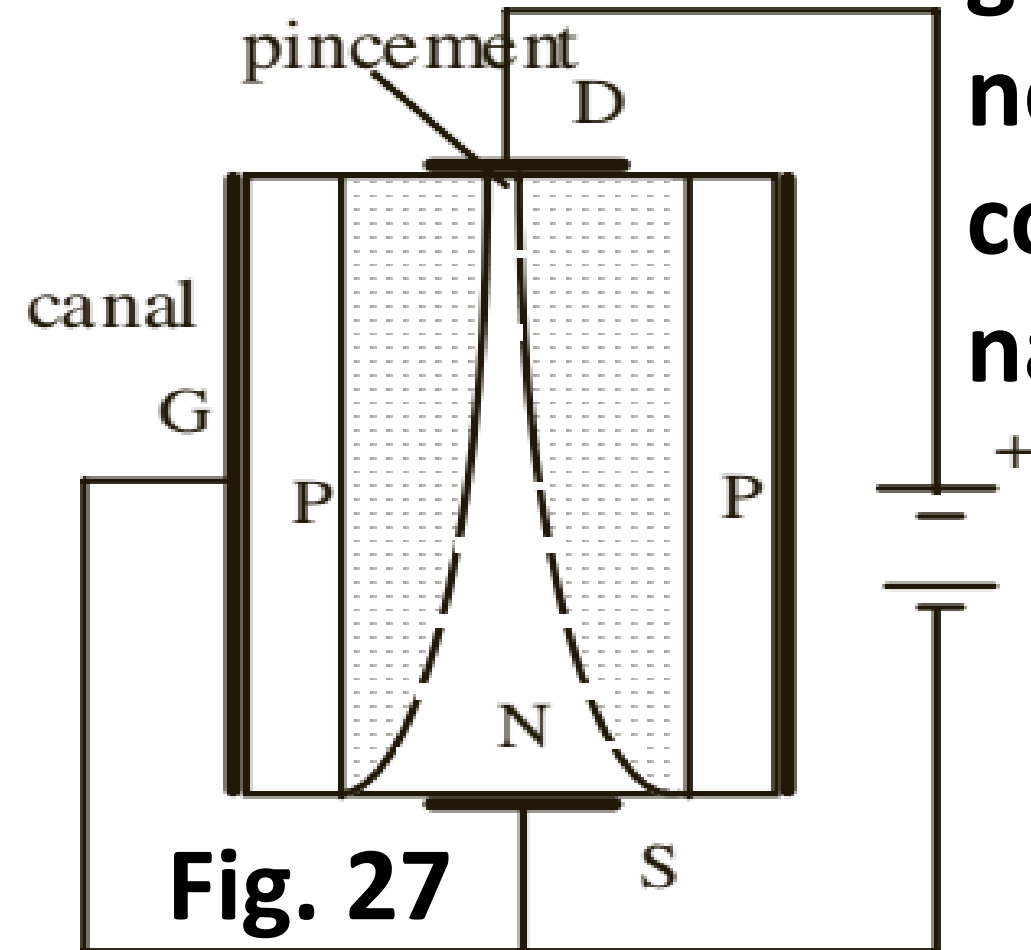Junction field effect transistor (FET) working of JFET



gate voltage becomes more negative, depletion layers expand, conducting channel becomes narrower

V_{GS} is negative enough, depletion layers touch, drain current is cut off

Fig. 27

Transistors: focused FETs

Junction field effect transistor (FET) working of JFET

gate voltage becomes more negative, depletion layers expand, conducting channel becomes narrower

V_{GS} is negative enough, depletion layers touch, drain current is cut off

Transistors: focused FETs

Junction field effect transistor (FET) working of JFET

$$U_{DS} = U_{DG} + U_{GS} = -U_{GD} + U_{GS} \quad \text{Eq.(10)}$$

$$U_{GS} = 0, \quad U_{DS} = -U_P + 0 = -U_P (U_{DS} > 0) \quad \text{Eq.(11)}$$